

The Ideal Power Distribution Network

YOUR BEST POWER INTEGRITY DESIGN WILL BE YOUR NEXT ONE

Heidi Barnes

2019.08.21

SI/PI Applications Engineer / Keysight Technologies



Agenda

- **Overview of current design and test trends**
- Power delivery network complexity
- Power rail impedance finds worst case failures
- Target impedance and root cause of ringing on power rail
- Designing for flat impedance
- Power integrity workflow

Digital High Speed Electronics Are Everywhere




Smart Cities

**Every year, designers push new limits:
Faster data rates, lower power, smaller components, higher levels of
integration**



Smart Devices

 

Smart Compute




Smart Automotive




Smart Energy

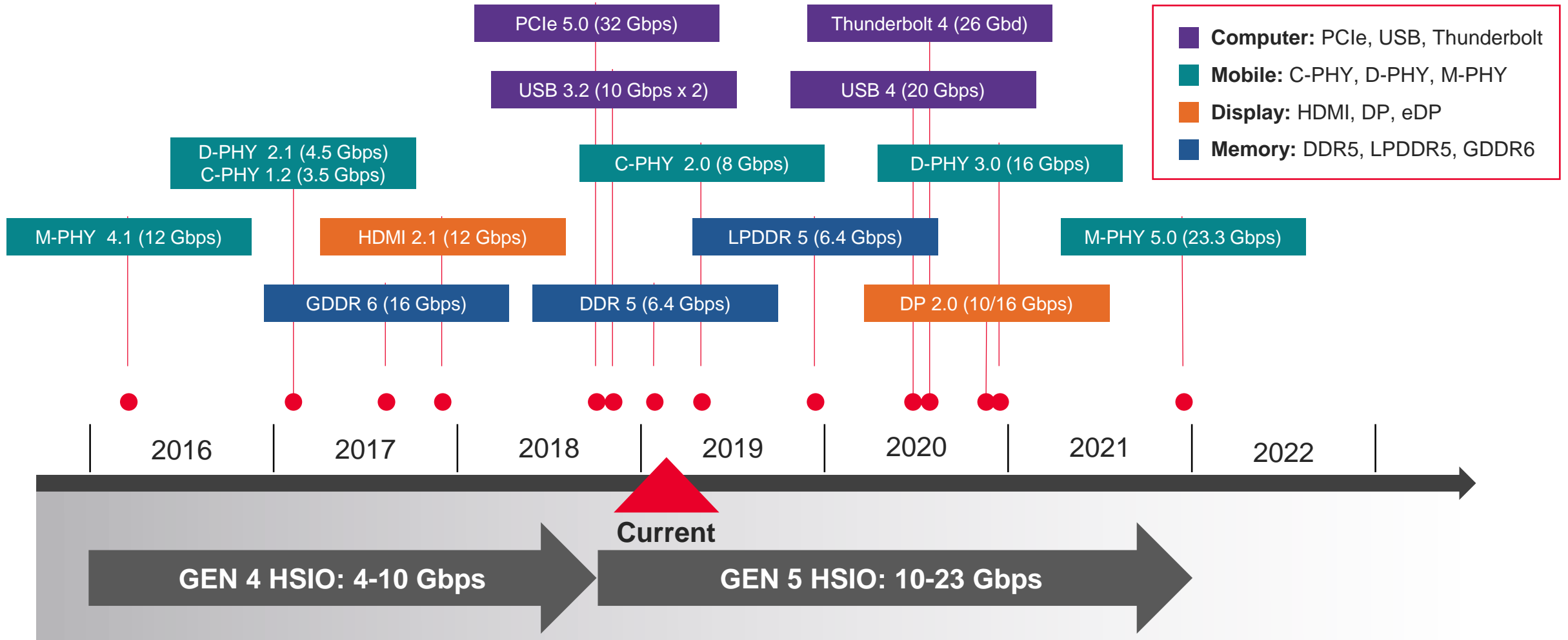Technology Waves Driving Higher Throughput



5G Networks Timeline

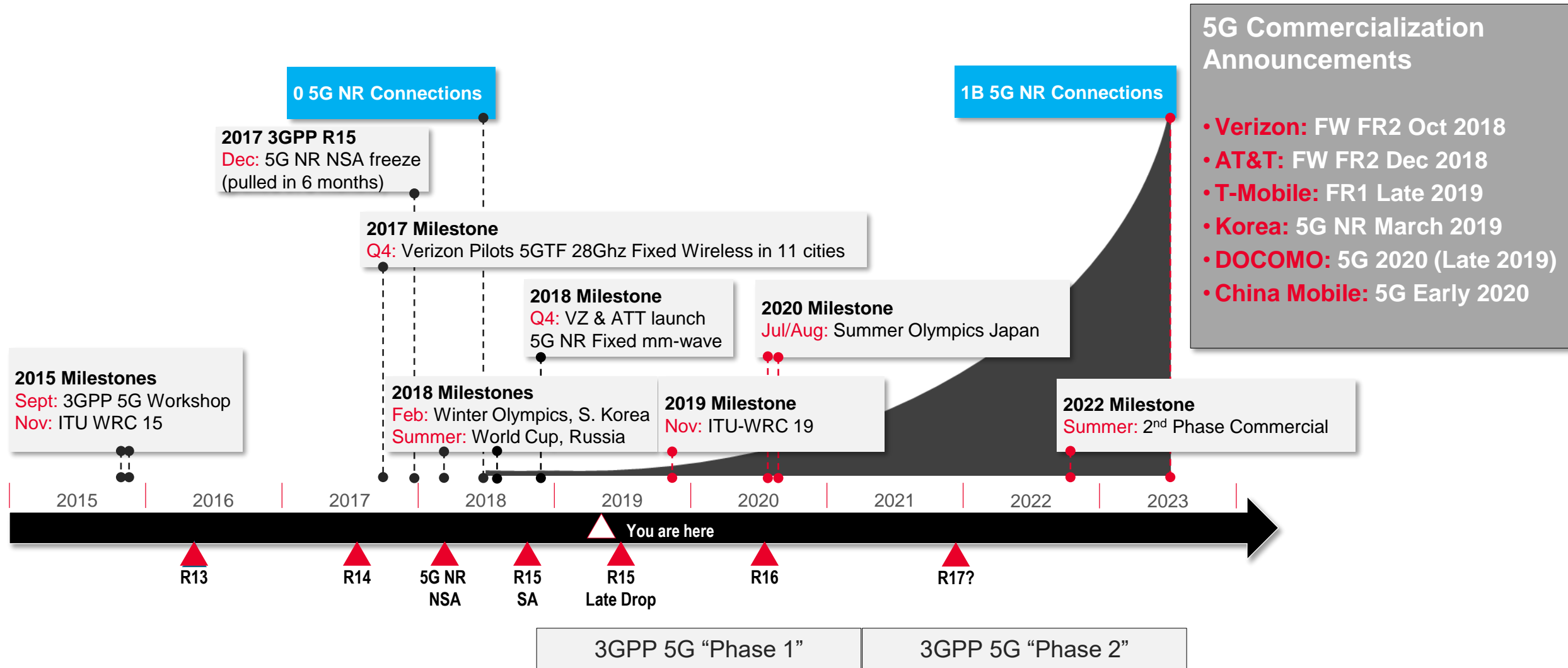

Design & Test Requirements are Growing Exponentially

5G NR

20x more
conformance tests
than 4G



Wireless Coexistence

Wi-Fi, *Bluetooth*®
GPS, FM Radio,
4G, 5G, NFC, RFID, Qi



EMI/EMC and Regulatory Test


20+
IEC & European (EN)
Standards



Failing EMI is Expensive



FINAL PRODUCT MUST PASS EMI/EMC REGULATIONS

Conducted Emission Testing

 

CISPR Compliance

  CISPR 25, Class 5 Compliance: Differential Noise (peak)




Agenda

- Overview of current design and test trends
- **Power delivery network complexity**
- Power rail impedance finds worst case failures
- Target impedance and root cause of ringing on power rail
- Designing for flat impedance
- Power integrity workflow

Electrical Schematics vs. Layout

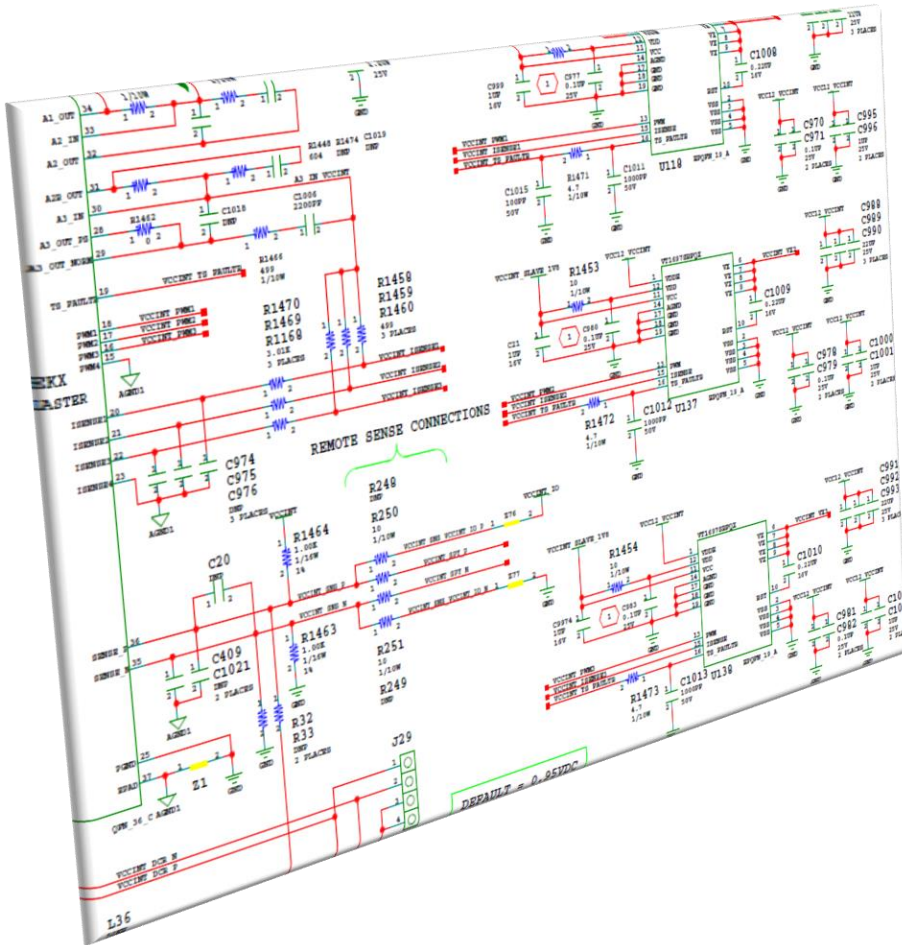POWER IS THE FOUNDATION THAT CONNECTS TO EVERYTHING




Modern High Density Electronics

- 1000s of nets
- A web of interconnected point of load power supplies
- 1 ground net
 - Barely noticeable on a schematic
 - Typically the largest copper net in layout
 - Noise path connected to everything

Power Integrity – Not Just DC

 FAST DELIVERY OF POWER AT MICROWAVE FREQUENCIES




Key Take Away:

Power Integrity Engineers need RF/uW design and measurement tools!

Power Delivery Eco-System

 - Many Point-of-Load power supplies
- Low Voltage, High $\frac{dI}{dt}$ Switching Loads
- Target Z to reduce broadband $L \frac{dI}{dt}$ Voltage Noise
- Power Supply Rejection Ration (PSRR)
- DC-DC Converter Switching Noise and Stability



Note: A Point-of-Load (POL) Power Supply is typically a Switched Mode Power Supply (SMPS) with a Buck Regulator DC-DC Converter design that the Microprocessor PCB world often calls as a Voltage Regulator Module (VRM)


Old Methods Fail to Detect Worst Case Failures

DATA TX/RX FAILURE, OVER VOLTAGE, EMI/EMC, CROSSTALK

$$V = L \frac{dI}{dt}$$

Old Method:
Step Load
Transient Test
(False Positive)

PASS
Datasheet
Design

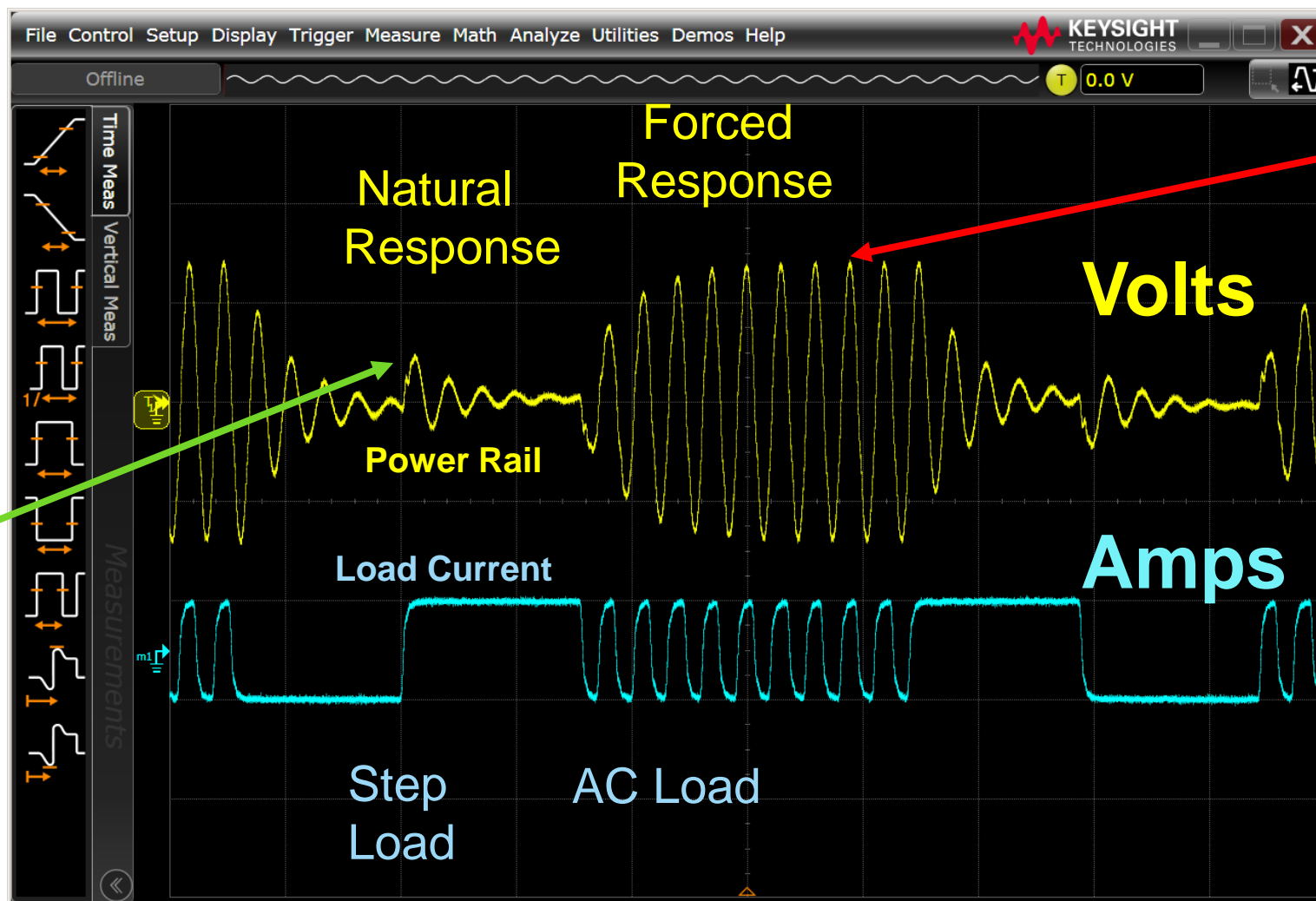

New Method:
Finding the
worst case Load

FAIL
Over Voltage
Tx/Rx Bit Error
EMI
Crosstalk

Key Take Away:
Forced response *is*
worst case, not the
data sheet step load.

Agenda


- Overview of current design and test trends
- Power delivery network complexity
- **Power rail impedance finds worst case failures**
- Target impedance and root cause of ringing on power rail
- Designing for flat impedance
- Power integrity workflow

Power Rail Impedance is the New Way!


IMPEDANCE PEAKS IN THE FREQUENCY DOMAIN CAUSE POWER RAIL RIPPLE

$$V_{ripple} = I_{transient} * Z_{pdn}$$

 Impedance Peaks Help Predict Worst Case Load Transients




Forced Excitation at Peak Z Frequencies

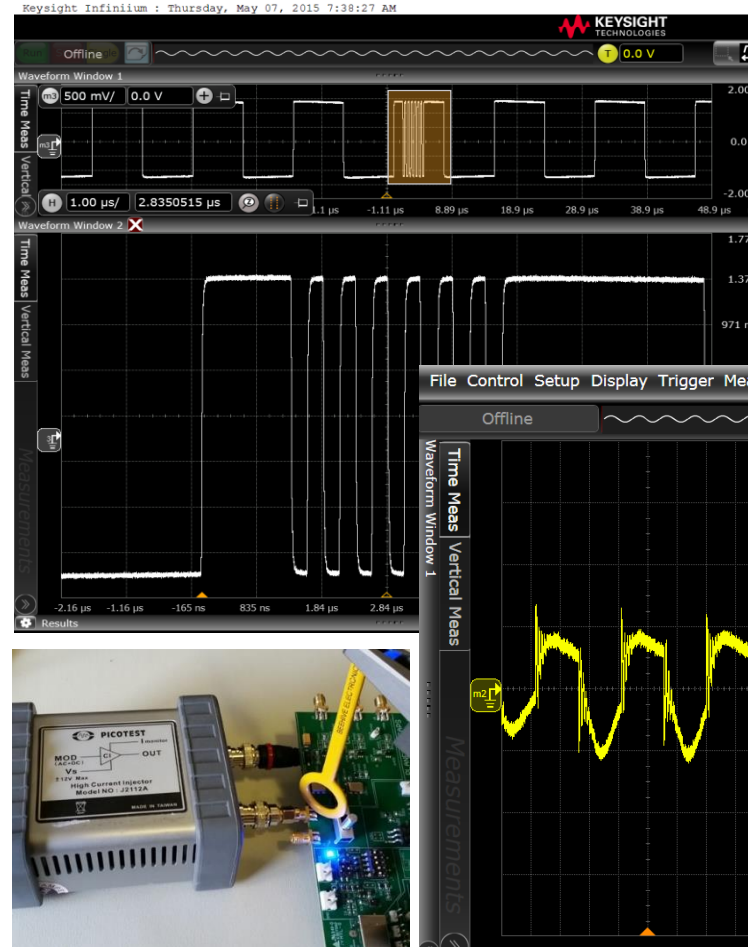

Key Take Away:
Voltage Rogue Waves are Real

Rogue Wave Captured


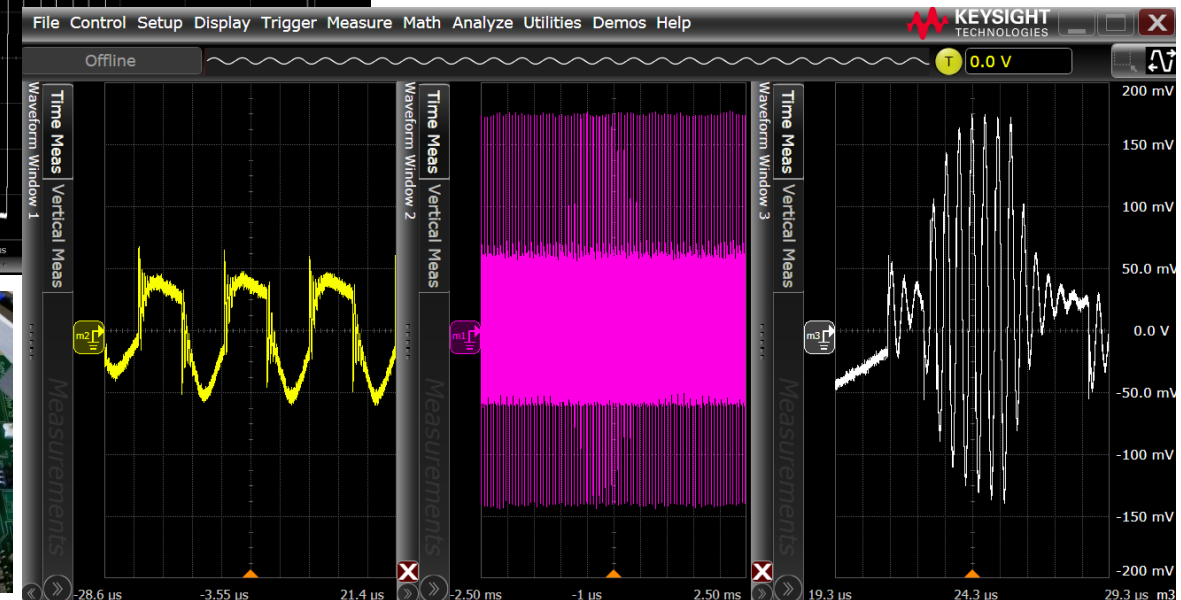


Target Z Keeps Getting Lower

FLAT Z DECOUPLING CAPACITOR OPTIMIZATION

- EM simulation and Measure Based Models Enable Low Z Designs
- Flat Z Optimization Lowers Cost, Reduces Risk of Failures, Maximizes Performance

High Density PCB Designs

  

Decoupling Capacitors

Yes	C190	330 uF
Yes	C215	330 uF
Yes	C216	330 uF
Yes	C218	330 uF
Yes	C303	220 nF
Yes	C305	220 nF
Yes	C750	220 nF
Yes	C753	220 nF
Yes	C757	220 nF

40% Fewer Components

Fewer solder joints higher reliability

No	C217	100 uF
No	C225	100 uF
No	C315	4.7 uF
No	C316	4.7 uF
No	C778	4.7 uF
No	C779	4.7 uF
No	C780	4.7 uF


Key Take Away:
Flat Z design over a wide bandwidth gives the best performance!

Agenda

- Overview of current design and test trends
- Power delivery network complexity
- Power rail impedance finds worst case failures
- **Target impedance and root cause of ringing on power rail**
- Designing for flat impedance
- Power integrity workflow

Power Integrity Target Impedance

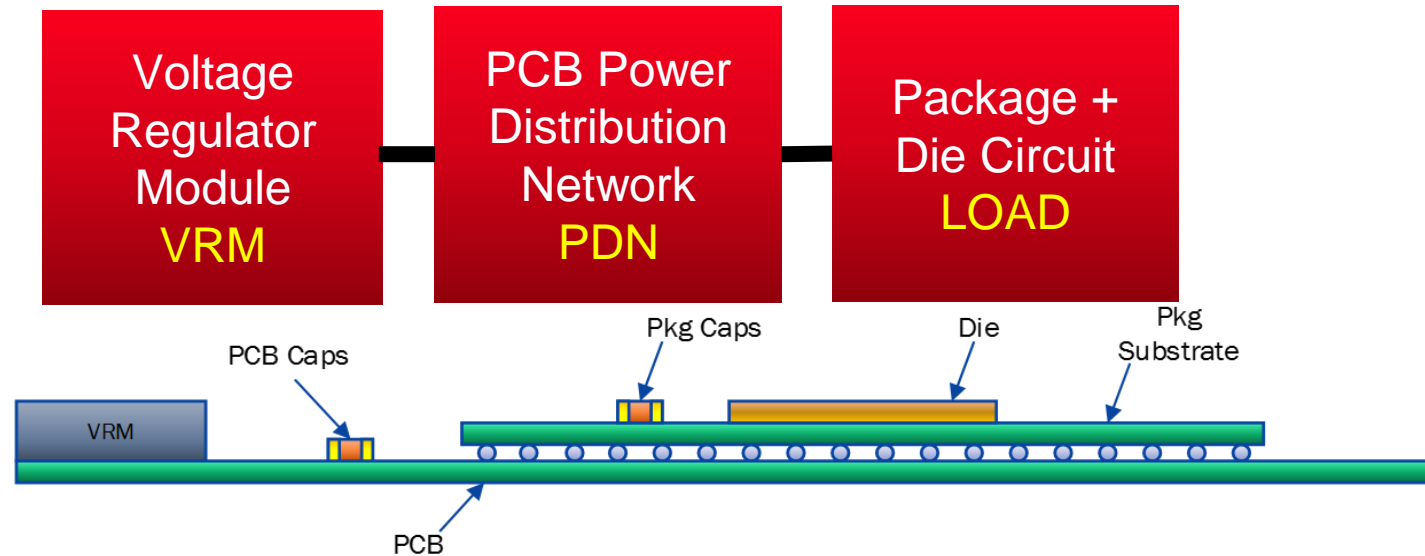TARGET Z TIMES DI/DT CURRENT TRANSIENT IS THE VOLTAGE RIPPLE



Target Impedance Calculation

$$Z_{\text{Target}} = \frac{\Delta V_{\text{Max Ripple}}}{\Delta I_{\text{Max Transient Load}}}$$


Where Does the Ringing Come From?

ENERGY SWINGS BETWEEN THE L AND THE C

*Energy stored in
the Magnetic Field*

$$V(t) = L \frac{di}{dt}$$

$$Z = j\omega L$$

 


Phase V Leads I


*Energy stored in
the Electric Field*

$$I = \int C \frac{dV}{dt}$$

$$Z = \frac{-1}{j\omega C}$$

 



Phase V Lags I

 

Root Cause of Ringing on the Power Rail

PARALLEL INDUCTANCE CAN RESONATE WITH THE DECOUPLING CAPACITANCE

Parallel L-C in the PDN

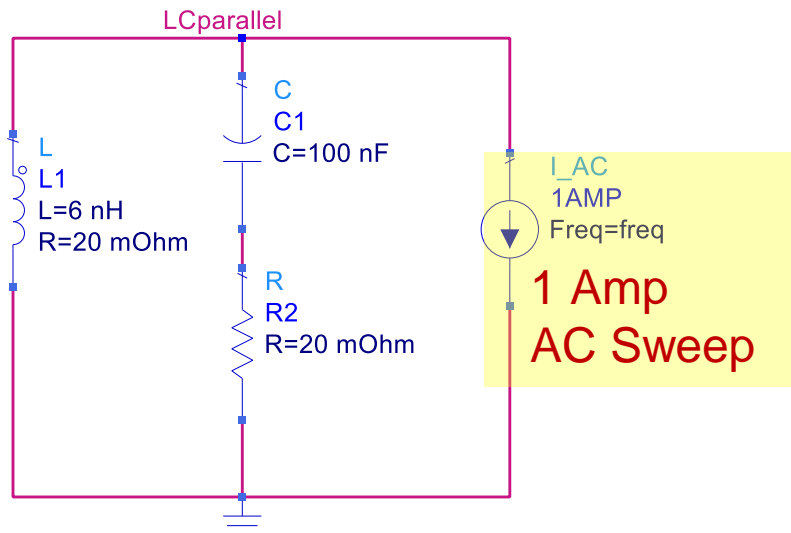 

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$


$$\Delta V = \Delta I \cdot Z_{peak}$$

$$Z_{peak} = Z_0 \cdot Q$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$Q = \frac{Z_0}{R_{total}}$$

Impedance vs. Frequency

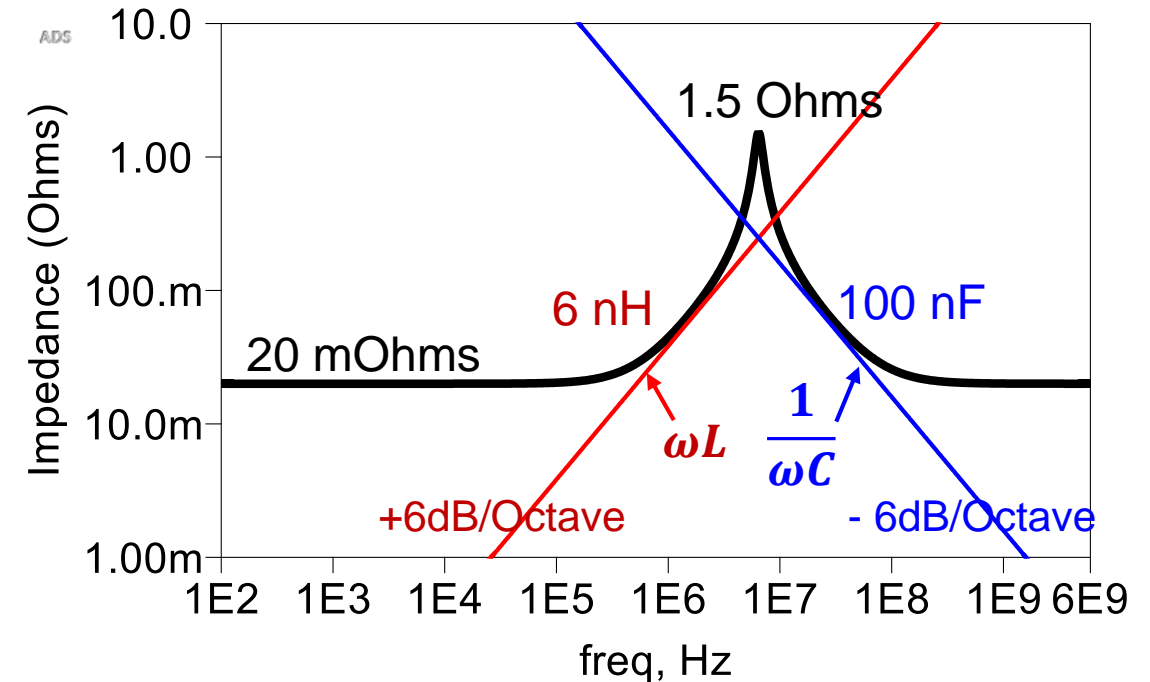

$$Z_{peak} = 1.5 \text{ Ohms}$$

$$Z_0 = 250 \text{ mOhms}$$

Agenda

- Overview of current design and test trends
- Power delivery network complexity
- Power rail impedance finds worst case failures
- Target impedance and root cause of ringing on power rail
- **Designing for flat impedance**
- Power integrity workflow

Bandwidth of the Power Supply Control Loop f_{supply}



DECOUPLING IS REQUIRED TO EXTEND THE POWER SUPPLY BANDWIDTH

PROBLEM

The Load can make the Power Supply Control Loop go unstable

1st Order SOLUTION

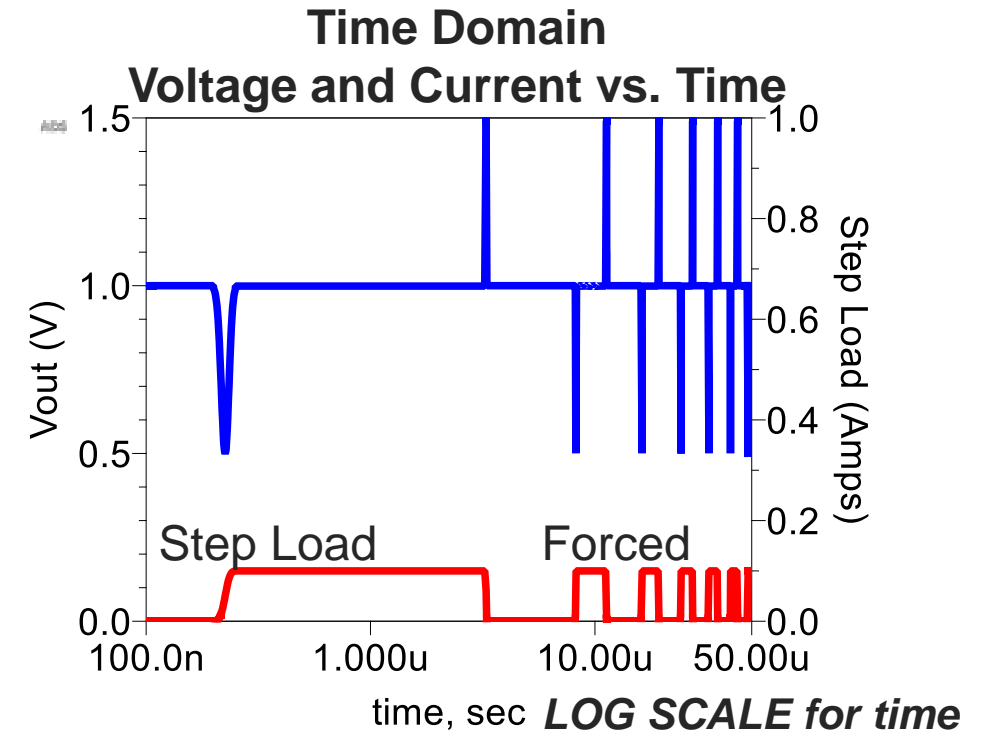 Design for Flat Impedance at the output to keep V and I in phase and the feedback stable.



Transition from Power Supply to Bulk Capacitor


DESIGNING FOR FLAT IMPEDANCE

PROBLEM

Find the decoupling capacitor that will maintain a Flat Z Load for the Power Supply


1st Order SOLUTION

 Add Bulk Capacitor to maintain flat impedance




$$C_{bulk} = \frac{L_{supply}}{Z_{Target}^2}$$

 Frequency Domain
Power Supply Output Impedance




Time Domain
Voltage and Current vs. Time

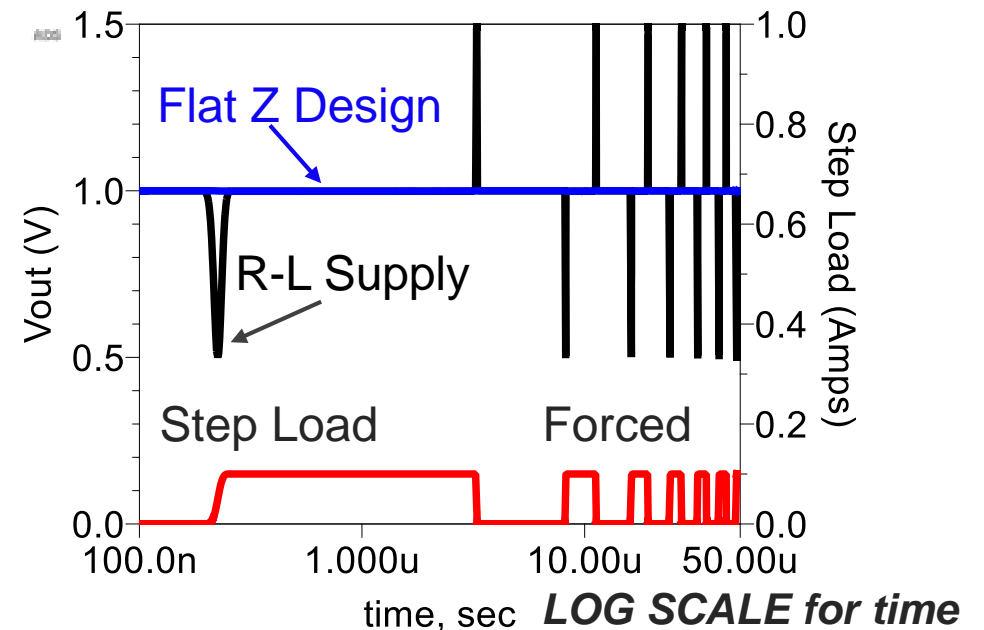

Capacitors Have Series L and Series R

SELECT ESR FOR FLAT Z PDN, MINIMIZE THE ESL

Capacitor Model

 


Impedance Equation

$$Z = R_{cap} + \left(j\omega L_{cap} - j\frac{1}{\omega C} \right)$$

$$f_{cap} = \frac{1}{2\pi\sqrt{L_{cap} \times C}}$$

Voltage and current are in phase at f_{cap}



Series RLC Impedance vs. Frequency

 

Adding Decoupling Capacitors to Reduce L

SMALLER CAPACITORS HAVE LOWER ESL

  Frequency Domain
Power Supply Output Impedance




$$C_{decap2} = \frac{L_{decap1}}{Z_{Target}^2}$$

$$= \frac{875pH}{(24 mOhm)^2}$$

$$\approx 1.5 \mu F$$

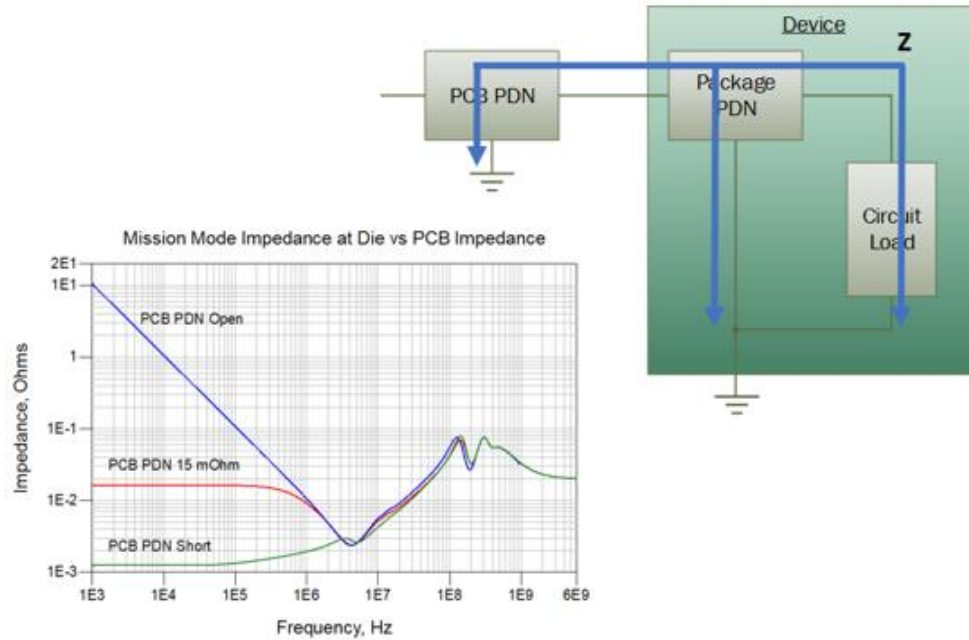
It's All About the Load and Noise Sources



Self-induced [inflicted] noise



Power Supply Noise Limits @ Package Ball
Power Supply Noise Spec: 10mV pk-pk

External [injected] noise

 



VRM + Load and No Decoupling Capacitors

  PARALLEL RESONANCE CAUSES AN IMPEDANCE PEAK



The Wrong Capacitor Can Add Parallel Resonances


INCREASES PART COUNT TO REACH TARGET Z

  


Flat Impedance PDN Design

FLAT Z = MAXIMUM STABILITY AND MINIMUM RIPPLE

 Frequency Domain
Impedance at the Package Pin




Time Domain
Voltage and Current vs. Time

 

History Lesson – The Transatlantic Cable

 ENGINEERED DESIGN VS. COSTLY DEBUG/REDESIGN



What is so hard about stringing a wire between the transmitter and the receiver?

Where was the SI Engineer in 1858?

Transatlantic telegraph cable

In 1858...signal quality declined rapidly, slowing transmission to an almost unusable speed. The cable was destroyed the following month when Wildman Whitehouse applied excessive voltage to it while trying to achieve faster operation.

Questions For Your Next Design

PI ENGINEERS REQUIRE SIMULATION AND MEASUREMENT TOOLS

1. Are your designs still leveraging decade capacitor values?
2. Are poor designs band-aided with added filters and more capacitors?
3. Where is the PI engineer?

Agenda


- Overview of current design and test trends
- Power delivery network complexity
- Power rail impedance finds worst case failures
- Target impedance and root cause of ringing on power rail
- Designing for flat impedance
- **Power integrity workflow**

Power Delivery Needs Simulation and Measurement

WHAT IS THE POWER INTEGRITY WORKFLOW?

Key Take Away:
The combined simulation and measurement of the PI Ecosystem reduces EMI/EMC failures

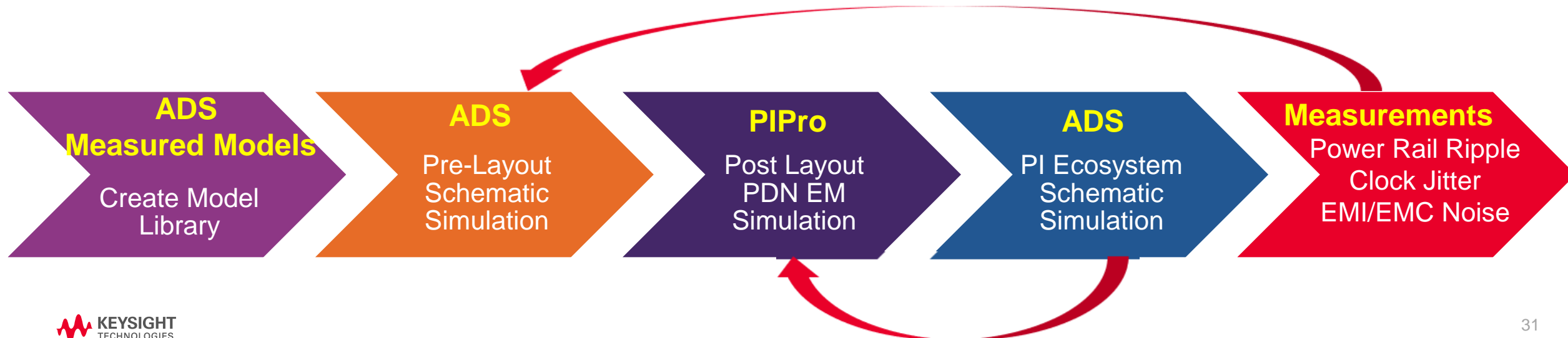- Designers often leverage designs and wait until **measurement** to debug
- Current industry workflow starts at **post-layout**, need to move to **pre-layout**
- Combined **power integrity** + **power electronics** covers both delivery and generation of power




Why the PI Workflow Needs EM Modeling


PDN EXAMPLE OF PARALLELING 5 CAPACITORS



Layout

 

EM Simulation with PIPro

 


EM Models Capture Real World PCB Parasitics


LUMPED SPICE MODEL GETS IT WRONG

Paralleling same value caps

	C	ESR	ESL
C1	1 uF	7 mΩ	300 pH

 

 Parallel Capacitors SPICE vs PCB EM Model




EM Models Capture Real World PCB Parasitics


Z AT THE LOAD IS NOT THE SAME AS Z AT THE VRM

Capacitor Loading by the Decade

	C	ESR	ESL
C1	1 uF	7 mΩ	300 pH
C2	0.10uF	15 mΩ	300 pH
C3	0.01uF	30 mΩ	300 pH
C4	0.001uF	100 mΩ	300 pH
C5	100pF	200 mΩ	300 pH

 

Z at Load vs. Z at VRM

 


PathWave ADS PIPro EM Simulation of the PCB PDN

EASY SETUP FOR HIGH PORT COUNT SIMULATIONS

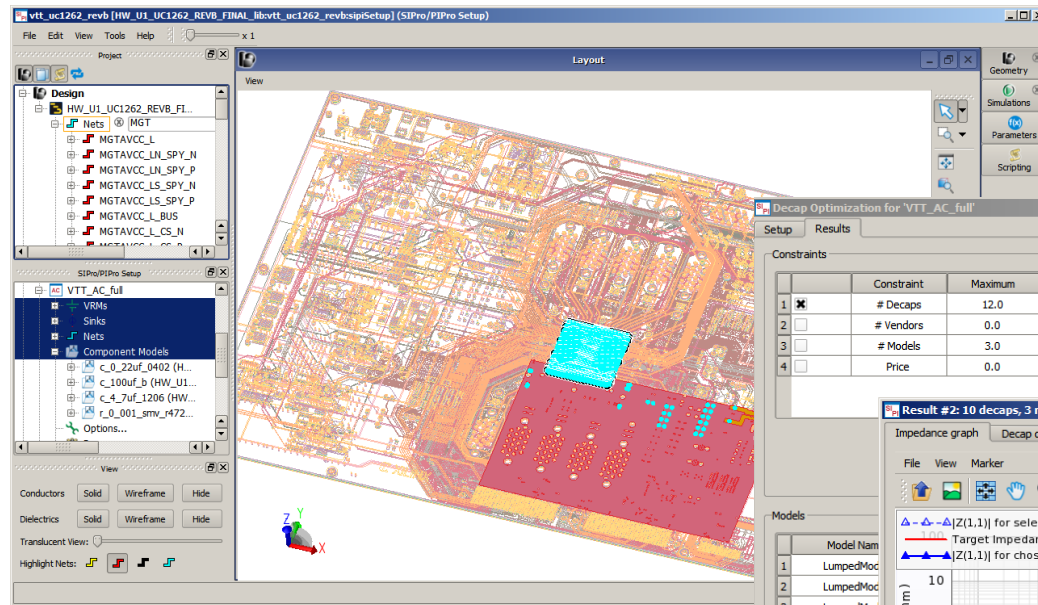
1) IMPORT THE PCB

- Select VRM, Sink, Nets, Components
- Run EM AC Frequency Sweep



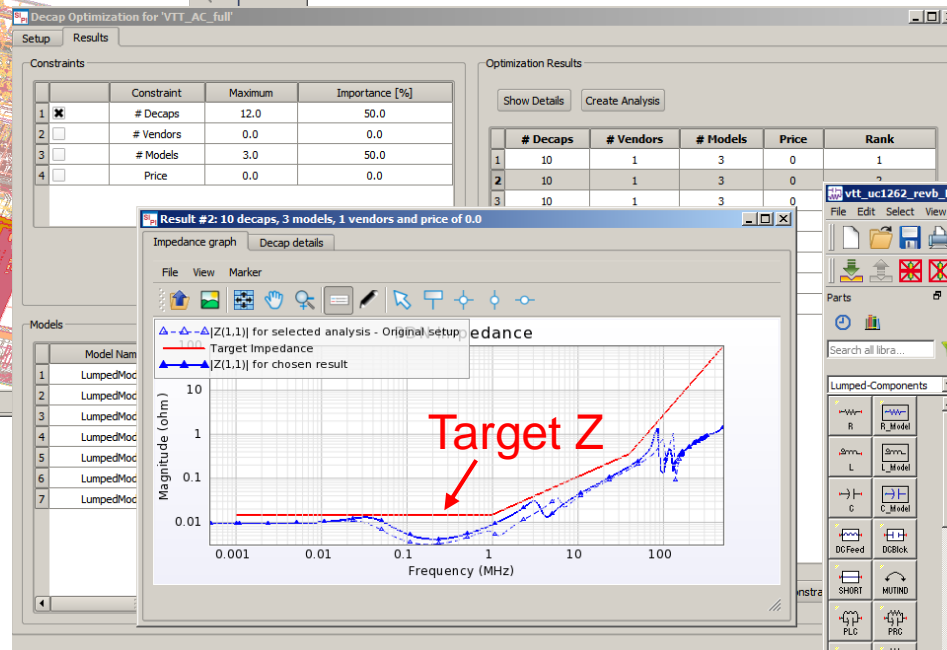
2) OPTIMIZE DECOUPLING

- Select capacitor models
- Setup optimization goals
- Run Optimization



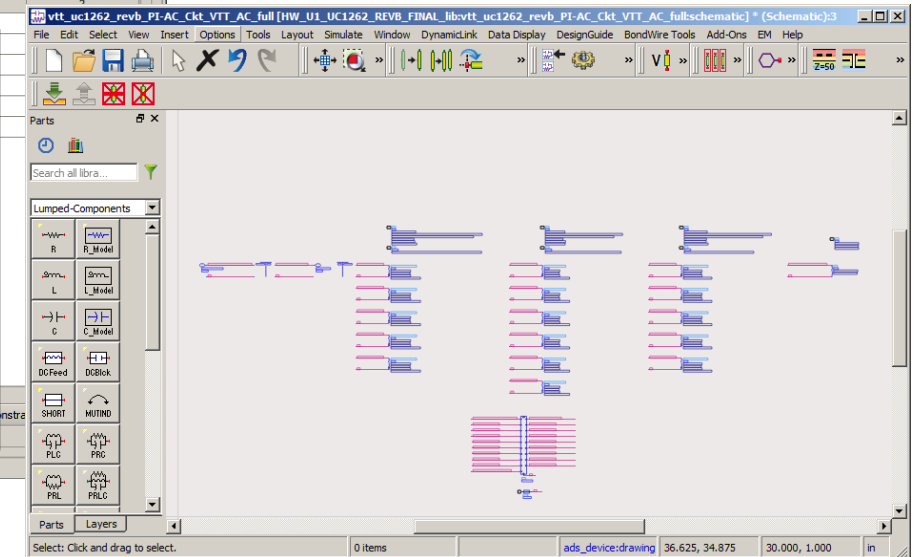2) GENERATE SCHEMATIC

- Auto generate schematic with PCB PDN EM model and optimized capacitors.




Voltage Regulator State Spaced Averaged Models

KEYSIGHT YOUTUBE VIDEO WITH PICOTEST


Measurement Based VRM Modeling

Steve Sandler – PICOTEST

 

How to Video

<http://tinyurl.com/vrm-video>

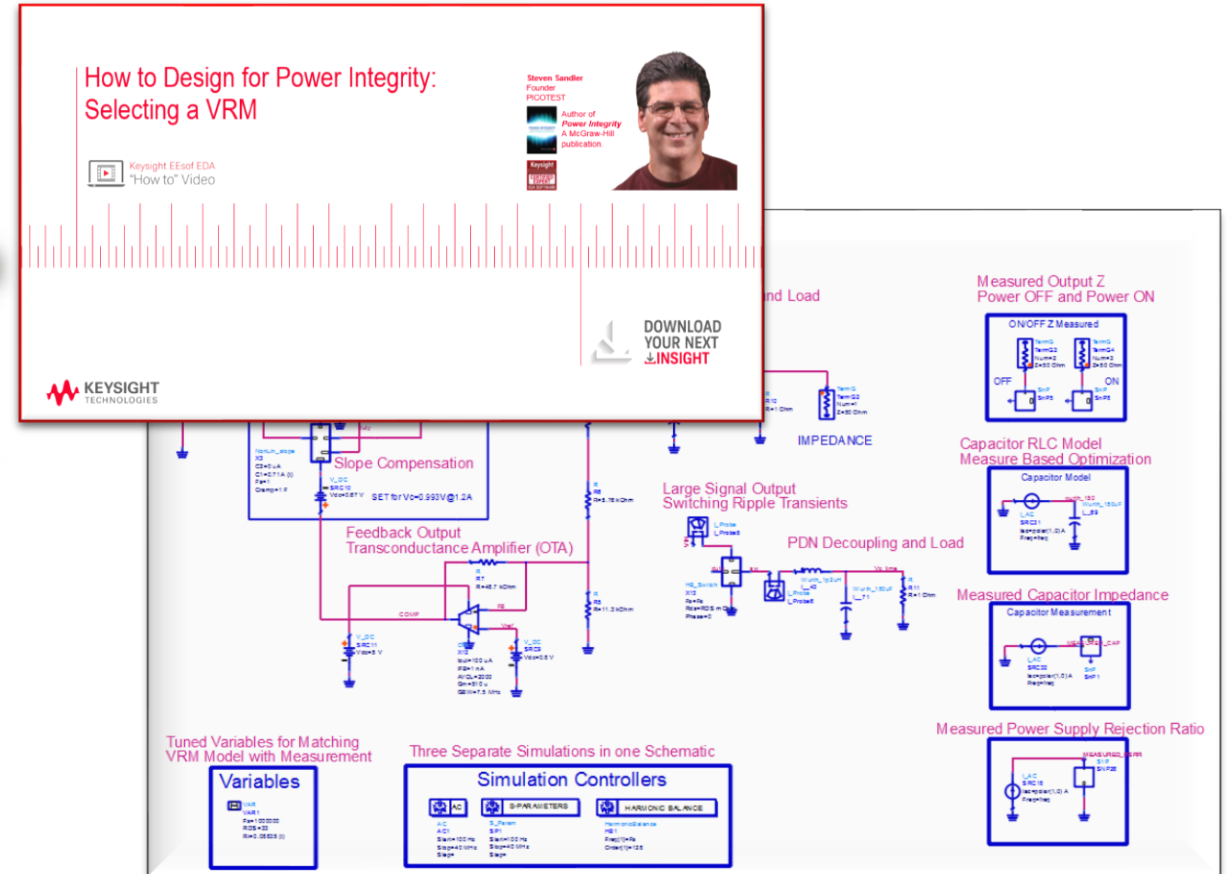

Modeling the Power Integrity Ecosystem

VRM + PDN + LOAD = PI ECOSYSTEM

Three Separate Simulations in one Schematic

Simulation Controllers



AC

AC1

Start=100 Hz
Stop=40 MHz
Step=



S Param

SP1

Start=100 Hz
Stop=40 MHz
Step=





HARMONIC BALANCE

HarmonicBalance

HB1

```
Freq[1]=Fs  
Order[1]=256
```

 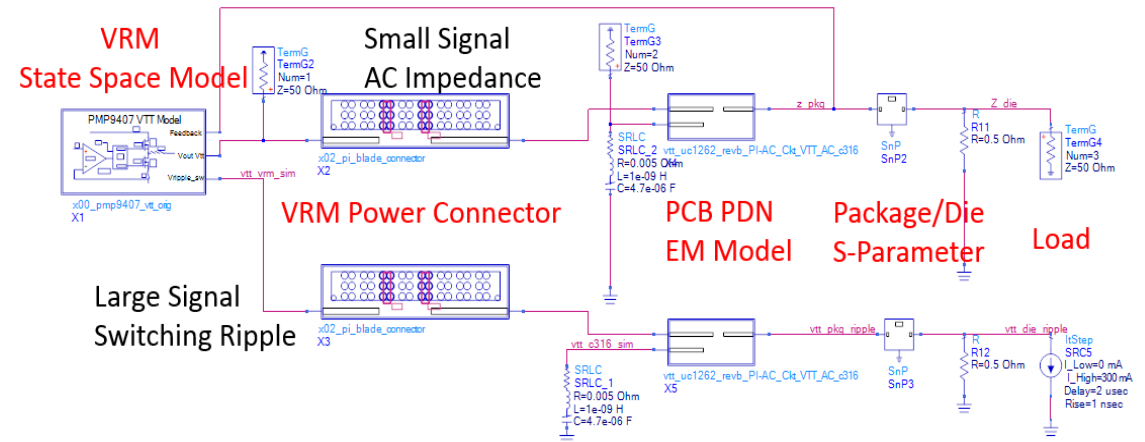


PI Simulation Demo with Harmonic Balance:

SMALL SIGNAL AC AND LARGE SIGNAL SWITCHING RIPPLE


ADS Schematic + Data Display

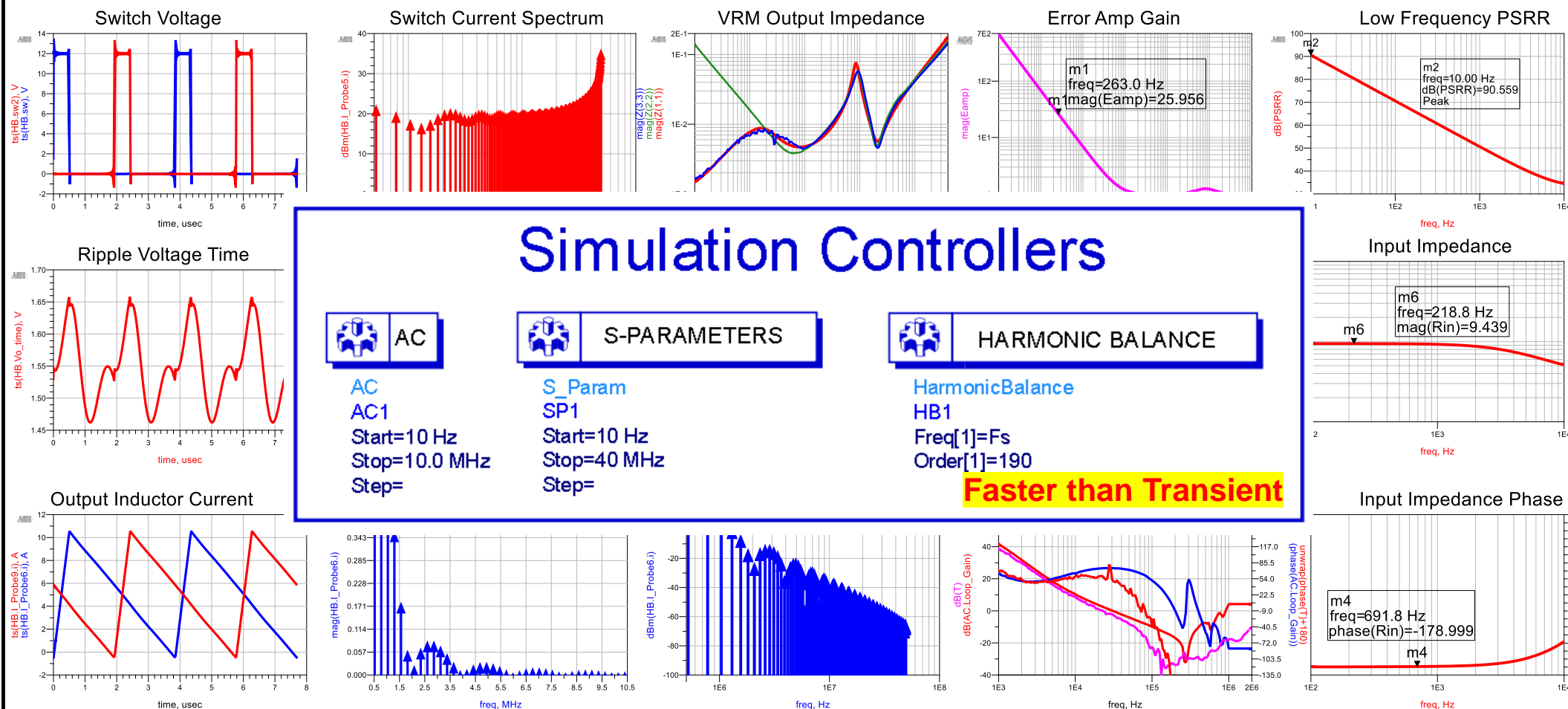Multi-phase DC-DC Converter State Space Hybrid Model - TPS40140




Power Integrity Simulation and Measurement Eco-System

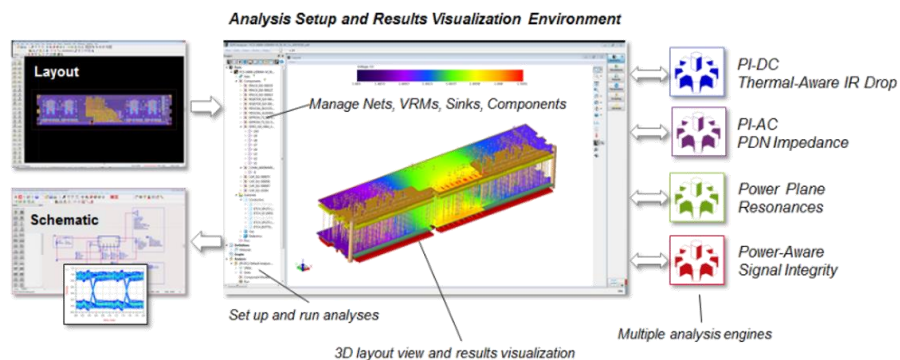PathWave ADS PIPro
EM Models for DeCap Optimization



 
E5061B for measuring
micro-Ohms of
Impedance




Picotest Accessories
PWR5061B PI Bundles



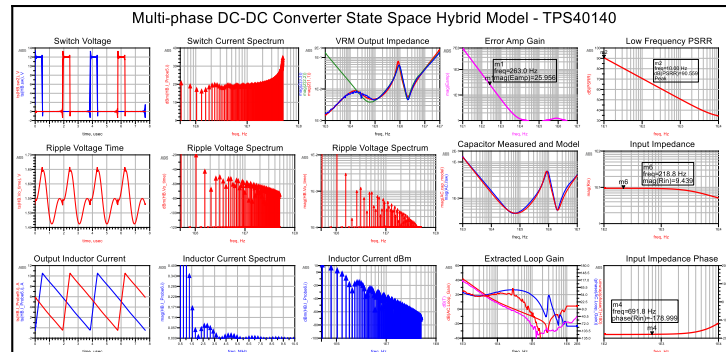
PathWave ADS PI Eco-System Simulations
Pre-Layout and Post Layout



 Infiniium Scope for Realtime
Power Rail Diagnostics



PE Next Generation GaN

 

Reaching for 99% Efficiency
MHz Switching
Doubling the Power Density
> 1000 W/in³

CX33000 Current Analyzer for
Load Transient Diagnostics



Summary

DESIGN METHODOLOGY FOR DECAP OPTIMIZATION

1. Calculate 1st order approximations

$$C_{bulk} = \frac{L_{supply}}{Z_{Target}^2} \quad C_{decap} = \frac{ESL_{Cbulk}}{Z_{Target}^2} \quad \text{Max } L_{PDN} = C_{pkg} * Z_{Target}^2$$

2. Decoupling capacitor optimization requires a Target Z input
3. Power Integrity Eco-System includes switching VRM models

How to Design for Power Integrity 5 Part Series on YouTube

with PI expert Steve Sandler

1

How to Design for Power Integrity:
Finding Power Delivery Noise Problems

Steven Sandler
Founder
PICOTEST
Author of
Power Integrity
A McGraw-Hill
publication.



Keysight EEsof EDA
"How to" Video

2

How to Design for Power Integrity:
Selecting a VRM

Steven Sandler
Founder
PICOTEST
Author of
Power Integrity
A McGraw-Hill
publication.



Keysight
"How to" Video

3

How to Design for Power Integrity:
Measuring, Modeling, Simulating
Capacitors and Inductors

Steven Sandler
Founder
PICOTEST
Author of
Power Integrity
A McGraw-Hill
publication.



Keysight EEsof EDA
"How to" Video

4

How to Design for Power Integrity:
DC-DC Converter Modeling and Simulation

Steven Sandler
Founder
PICOTEST
Author of
Power Integrity
A McGraw-Hill
publication.



Keysight EEsof EDA
"How to" Video

5

How to Design for Power Integrity:
Optimizing Decoupling Capacitors

Steven Sandler
Founder
PICOTEST
Author of
Power Integrity
A McGraw-Hill
publication.



Keysight EEsof EDA
"How to" Video

DOWNLOAD
YOUR NEXT
INSIGHT

Hands-On Lab 1b: 190219_PI_Lab1b_Load_wrk.7zads

Basics – Instructor Led Demo

Transceiver Turn-on with ideal R-L PCB PDN

Frequency Domain Impedance and Time Domain Excitation for ripple


Explore –

Package Model Impedance

Impedance at Package Pin vs. Die

Advanced –

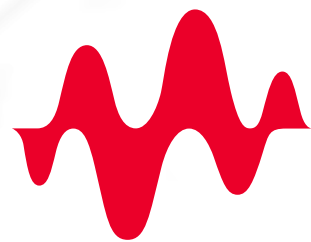Tune C_{total} for a given Target Z profile



KEYSIGHT
TECHNOLOGIES